1.

SOLUTION

(a) If the speed of rotation  $\omega$  of the shaft is 500 rad/s, then the voltage induced in the rotating loop will be

$$e_{ind} = 2rlB\omega$$
  
 $e_{ind} = 2(0.25 \text{ m})(0.5 \text{ m})(0.4 \text{ T})(500 \text{ rad/s}) = 50 \text{ V}$ 

Since the external battery voltage is only 48 V, this machine is operating as a generator, charging the battery.

(b) The current flowing out of the machine is approximately

$$i = \frac{e_{\text{ind}} - V_B}{R} = \left(\frac{50 \text{ V} - 48 \text{ V}}{0.4 \Omega}\right) = 5.0 \text{ A}$$

(Note that this value is the current flowing while the loop is under the pole faces. When the loop goes beyond the pole faces,  $e_{ind}$  will momentarily fall to 0 V, and the current flow will momentarily reverse. Therefore, the *average* current flow over a complete cycle will be somewhat less than 5.0 A.)

(c) If the speed of the rotor were increased to 550 rad/s, the induced voltage of the loop would increase to

$$e_{ind} = 2rlB\omega$$
  
 $e_{ind} = 2(0.25 \text{ m})(0.5 \text{ m})(0.4 \text{ T})(550 \text{ rad/s}) = 55 \text{ V}$ 

and the current flow out of the machine will increase to

$$i = \frac{e_{\text{ind}} - V_B}{R} = \left(\frac{55 \text{ V} - 48 \text{ V}}{0.4 \Omega}\right) = 17.5 \text{ A}$$

(d) If the speed of the rotor were decreased to 450 rad/s, the induced voltage of the loop would fall to

$$e_{\text{ind}} = 2rlB\omega$$
  
 $e_{\text{ind}} = 2(0.25 \text{ m})(0.5 \text{ m})(0.4 \text{ T})(450 \text{ rad/s}) = 45 \text{ V}$ 

Here,  $e_{ind}$  is less than  $V_B$ , so current flows into the loop and the machine is acting as a motor. The current flow into the machine would be

$$i = \frac{V_B - e_{ind}}{R} = \left(\frac{48 \text{ V} - 45 \text{ V}}{0.4 \Omega}\right) = 7.5 \text{ A}$$

2.

SOLUTION From the DC test,

$$2R_{\rm l} = \frac{13.5 \text{ V}}{64 \text{ A}} \qquad \Rightarrow \qquad R_{\rm l} = 0.105 \,\Omega$$

$$-\frac{I_{\rm DC}}{+}$$

$$V_{\rm DC}$$

$$R_{\rm l} = \frac{13.5 \, \text{V}}{64 \, \text{A}} \qquad \Rightarrow \qquad R_{\rm l} = 0.105 \,\Omega$$

In the no-load test, the line voltage is 208 V, so the phase voltage is 120 V. Therefore,

$$X_1 + X_M = \frac{V_\phi}{I_{Anl}} = \frac{120 \text{ V}}{24.0 \text{ A}} = 5.00 \Omega$$
 @ 60 Hz

In the locked-rotor test, the line voltage is 24.6 V, so the phase voltage is 14.2 V. From the locked-rotor test at 15 Hz,

$$\begin{aligned} |Z'_{LR}| &= |R_{LR} + jX'_{LR}| = \frac{V_{\phi}}{I_{A,LR}} = \frac{14.2 \text{ V}}{64.5 \text{ A}} = 0.220 \text{ }\Omega \\ \theta'_{LR} &= \cos^{-1} \frac{P_{LR}}{S_{LR}} = \cos^{-1} \left[ \frac{2200 \text{ W}}{\sqrt{3} (24.6 \text{ V}) (64.5 \text{ A})} \right] = 36.82^{\circ} \end{aligned}$$

Therefore,

$$\begin{split} R_{\text{LR}} &= \left| Z'_{\text{LR}} \right| \; \cos \theta_{\text{LR}} = (0.220 \; \Omega) \cos \left( 36.82^{\circ} \right) = 0.176 \; \Omega \\ \Rightarrow & \; R_1 + R_2 = 0.176 \; \Omega \\ \Rightarrow & \; R_2 = 0.071 \; \Omega \\ X'_{\text{LR}} &= \left| Z'_{\text{LR}} \right| \; \sin \theta_{\text{LR}} = \left( 0.2202 \; \Omega \right) \sin \left( 36.82^{\circ} \right) = 0.132 \; \Omega \end{split}$$


At a frequency of 60 Hz,

$$X_{LR} = \left(\frac{60 \text{ Hz}}{15 \text{ Hz}}\right) X'_{LR} = 0.528 \Omega$$

For a Design Class B motor, the split is  $\,X_1 = 0.211\,\Omega\,$  and  $\,X_2 = 0.317\,\Omega\,$  . Therefore,

$$X_M = 5.000 \ \Omega - 0.211 \ \Omega = 4.789 \ \Omega$$

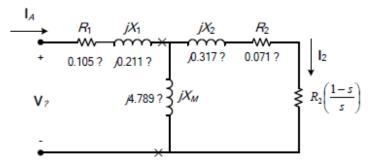The resulting equivalent circuit is shown below:



A MATLAB program to calculate the torque-speed characteristic of this motor is shown below:

```
% M-file: prob6_20.m
% M-file create a plot of the torque-speed curve of the
% induction motor of Problem 6-20.
% First, initialize the values needed in this program.
r1 = 0.105;
                            % Stator resistance
x1 = 0.211;
                            % Stator reactance
r2 = 0.071;
                            % Rotor resistance
                            % Rotor reactance
x2 = 0.317;
xm = 4.789;
                            % Magnetization branch reactance
v phase = 208 / sqrt(3);
                           % Phase voltage
n_sync = 1200;
                            % Synchronous speed (r/min)
w_{sync} = 125.7;
                            % Synchronous speed (rad/s)
% Calculate the Thevenin voltage and impedance from Equations
% 6-41a and 6-43.
r_th = real(z_th);
x_{th} = imag(z_{th});
% Now calculate the torque-speed characteristic for many
% slips between 0 and 1. Note that the first slip value
% is set to 0.001 instead of exactly 0 to avoid divide-
% by-zero problems.
s = (0:1:50) / 50;
                            % Slip
s(1) = 0.001;
nm = (1 - s) * n_sync;
                             % Mechanical speed
% Calculate torque versus speed
for ii = 1:51
   t ind(ii) = (3 * v th^2 * r2 / s(ii)) / ...
           (w \text{ sync } * ((r \text{ th} + r2/s(ii))^2 + (x \text{ th} + x2)^2));
% Plot the torque-speed curve
figure(1);
plot(nm,t_ind,'b-','LineWidth',2.0);
xlabel('\bf\itn_{m}');
ylabel('\bf\tau_{ind}');
title ('\bfInduction Motor Torque-Speed Characteristic');
```

grid on;

The resulting plot is shown below:

