

(1)

A three-phase Y- $\Delta$  transformer is rated 225-kV:24-kV (line to line), 400 MVA and has a single-phase equivalent series reactance of  $6.08\Omega$  (as referred to its high-voltage terminals).

The transformer is supplying a load of 375 MVA at 0.89 power factor leading at a voltage of 24 kV (line to line) on its low-voltage side. It is supplied from a feeder whose impedance is  $0.17 + j2.2\Omega$  (connected to its high-voltage terminals).

For these conditions, calculate

- (a) the line-to-line voltage at the high-voltage terminals of the transformer
- (b) the line-to-line voltage at the sending end of the feeder.