

(1)

A three-phase Y- $\Delta$  transformer is rated 225-kV:24-kV (line to line), 400 MVA and has a single-phase equivalent series reactance of  $6.08\Omega$  (as referred to its high-voltage terminals).

The transformer is supplying a load of 375 MVA at 0.89 power factor leading at a voltage of 24 kV (line to line) on its low-voltage side. It is supplied from a feeder whose impedance is  $0.17 + j2.2\Omega$  (connected to its high-voltage terminals).

For these conditions, calculate

- (a) the line-to-line voltage at the high-voltage terminals of the transformer
- (b) the line-to-line voltage at the sending end of the feeder.

## Homework 5

$$(a) \quad U_L = \frac{24 \text{ kV}}{\sqrt{3}} = 13.86 \text{ kV}$$

$$I_L = \frac{317 \text{ MVA}}{\sqrt{3} \cdot 24 \text{ kV}} e^{j\phi} = 9.021 e^{j\phi} \text{ kA}$$

$$\phi = \cos^{-1} 0.89 = 27.12^\circ$$

$$\text{Turn ratio } N = \frac{225}{24} = 9.375$$

$$\therefore U_L' = N U_L = 9.375 \times 13.86 = 129.9 \text{ kV}$$

$$I_L' = \frac{I_L}{N} = \frac{9.021 e^{j\phi}}{9.375} = 0.9622 e^{j\phi} \text{ kA}$$

High-side line neutral terminal voltage:

$$U_H = |U_L' + j X_t I_L'| = |129.9 + j 6.08 \times 0.9622 \angle 27.12^\circ| = 127.3 \text{ kV}$$

Line-line voltage:

$$\sqrt{3} \times 127.3 = 220.49 \text{ kV}$$

$$(b) \quad U_S = |U_L' + (Z_f + j X_t) I_L'| = |129.9 + (0.17 + j 2.2) \cdot 6.08 \cdot 0.9622 \angle 27.12^\circ| = 125.5 \text{ kV}$$

Line-line voltage:

$$\sqrt{3} \times 125.5 = 217.4$$