

(1)

A 100-kVA 8000/277-V distribution transformer has the following resistances and reactances:

$$R_p = 5 \, \Omega \qquad R_s = 0.005 \, \Omega$$

$$X_p = 6 \, \Omega \qquad X_s = 0.006 \, \Omega$$

$$R_c = 50 \, \text{k}\Omega \qquad X_M = 10 \, \text{k}\Omega$$

The excitation branch impedances are given referred to the high-voltage side of the transformer.

(The values on the nameplate are rated line voltage and line current)

- (a) Find the equivalent circuit of this transformer referred to the low-voltage side.
- (b) Assume that this transformer is supplying rated load at 277 V and 0.85 PF lagging. What is this transformer's input voltage? What is its voltage regulation?
- (c) What are the copper losses and core losses in this transformer under the conditions of part (b)?
- (d) What is the transformer's efficiency under the conditions of part (b)?

(2)

The nameplate on a 25-MVA, 60-Hz single-phase transformer indicates that it has a voltage rating of 8.0-kV:78-kV. A short-circuit test from the high-voltage side (low-voltage winding short circuited) gives readings of 4.53 kV, 321 A, and 77.5 kW. An open-circuit test is conducted from the low-voltage side and the corresponding instrument readings are 8.0 kV, 39.6 A, and 86.2 kW.

- a. Calculate the equivalent series impedance of the transformer as referred to the high-voltage terminals.
- b. Calculate the equivalent series impedance of the transformer as referred to the low-voltage terminals.