

A 25-MVA, 12.2-kV, 0.9-PF-lagging, three-phase, two-pole, Y-connected, 60-Hz synchronous generator was tested by the open-circuit test, and its air-gap voltage was extrapolated with the following results:

Open-circuit test

Field current, A	275	320	365	380	475	570
Line voltage, kV	12.2	13.0	13.8	14.1	15.2	16.0
Extrapolated air-gap voltage, kV	13.3	15.4	17.5	18.3	22.8	27.4

The short-circuit test was then performed with the following results:

Short-circuit test

Field current, A	275	320	365	380	475	570
Armature current, A	890	1040	1190	1240	1550	1885

The armature resistance is $0.6\ \Omega$ per phase.

- Find the unsaturated synchronous reactance of this generator in ohms per phase and in per-unit.
- Find the approximate saturated synchronous reactance X_s at a field current of 380 A. Express the answer both in ohms per phase and in per-unit.
- Find the approximate saturated synchronous reactance at a field current of 475 A. Express the answer both in ohms per phase and in per-unit.
- Find the short-circuit ratio for this generator.
- What is the internal generated voltage of this generator at rated conditions?
- What field current is required to achieve rated voltage at rated load?

Homework 9

(a) Phase voltage : $V_{\phi} = \frac{12.2}{\sqrt{3}} = 7.044 \text{ kV}$

$$V_{\phi-\text{ag}} = \frac{13.3}{\sqrt{3}} = 7.679 \text{ kV}$$

$$X_{su} = \frac{V_{\phi-\text{ag}}}{I_{a, \text{sc}}} = \frac{7.679 \times 10^3}{890} = 8.628 \Omega$$

$$Z_{\text{base}} = \frac{\sqrt{3} V_{\phi-\text{base}}^2}{S} = \frac{3 \times (7044)^2}{25 \times 10^6} = 5.954 \Omega$$

↓

$$X_{su, \text{pu}} = \frac{8.628}{5.954} = 1.449$$

(b) $X_s = \frac{V_{\phi'}}{I_{a'}} = \frac{\frac{14.1 \times 10^3}{\sqrt{3}}}{1240} = 6.505 \Omega$

per-unit : $X_{s, \text{pu}} = \frac{6.505}{5.954} = 1.0925$

(c) $X_s = \frac{V_{\phi''}}{I_{a''}} = \frac{\frac{15.2 \times 10^3}{\sqrt{3}}}{1550} = 5.662 \Omega$

per-unit : $X_{s, \text{pu}} = \frac{5.662}{5.954} = 0.9509$

(d) O-C test : $12.2 \text{ kV} \rightarrow 275 \text{ A}$

$$I_L = \frac{25 \times 10^6}{\sqrt{3} \times (12.2 \times 10^3)} = 1183 \text{ A} \quad \Rightarrow \quad \text{SCR} = \frac{275}{365} = 0.75$$

↳ S-C test : $1183 \text{ A} \rightarrow 365 \text{ A}$

(e) $\cos^{-1}(0.9) = 25.84^\circ$, lagging

$$\vec{E}_A = \vec{V}_{\phi} + \vec{I}_A (R_A + jX_s)$$

$$\therefore \vec{I}_A = 1183 \angle -25.84^\circ$$

$$\Rightarrow = 7044 \angle 0^\circ + 1183 \angle -25.84^\circ (0.6 + j6.505)$$

$$\vec{V}_{\phi} = 7.044 \text{ kV} \angle 0^\circ$$

$$= 12868 \angle 30.94^\circ$$

$$(f) \quad \text{Line voltage: } 12868 \times \sqrt{3} = 22288 \text{ V}$$

$$I_a: 22.288 \text{ kV} \rightarrow 475 \text{ A}$$