

第5次习题课

- 恒定激励作用下高阶电路的求解

- 二阶

- 状态方程

- 任意激励作用下任意阶电路的求解

- 单位冲激响应

- 卷积积分

- 强制换路 \leftrightarrow 电荷守恒/磁链守恒

- 为确保KCL/KVL成立，必须电感电流/电容电压跳变，进而产生的冲激电压/冲激电流

- 和L12中冲激电源产生的电感电流/电容电压跳变不一样

记忆：

RLC串联二阶的特征方程

$$p^2 + \frac{R}{L}p + \frac{1}{LC} = 0$$

单选题 1分

满足 $q=Cu$ 定义式的电容 C 为

- ☒ A 线性电容
- ☐ B 非线性电容
- ☐ C 不好说

$\underline{u=RI}$	$u=f(i)$	$i=g(u)$
$\underline{q=Cu}$	$q=f(u)$	$u=g(q)$
$\underline{\varphi=Li}$	$\varphi=f(i)$	$i=g(\varphi)$

单选题 1分


由线性电阻、线性电容和独立源构成的电路为

- ☒ A 线性电路
- ☐ B 非线性电路
- ☐ C 不好说

单选题 1分

非零状态下，线性电容的 u - i 积分关系为

- ☒ A 线性关系
- ☐ B 非线性关系
- ☐ C 不好说

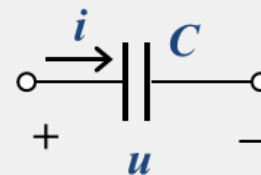

$$u(t) = u(0) + \frac{1}{C} \int_0^t i d\tau$$

$$y = ax + b$$

单选题 1分


非零状态下，由线性电阻、线性电容和独立源构成的电路为

- ☒ A 线性电路
- ☐ B 非线性电路
- ☐ C 不好说

单选题 1分

该电路为

- ☒ A 过阻尼
- ☐ B 临界阻尼
- ☐ C 欠阻尼
- ☐ D 无阻尼

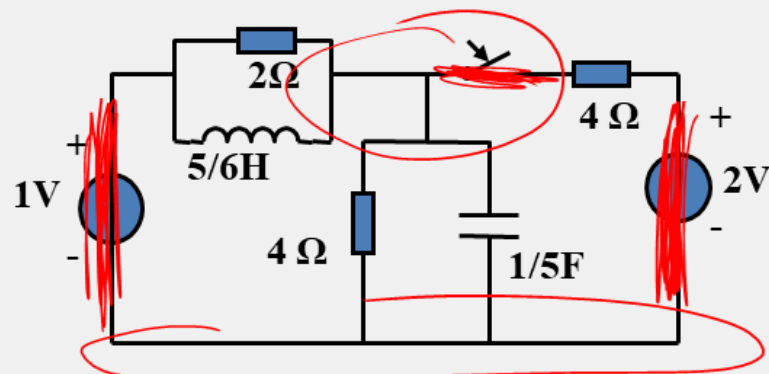


$$R = 1 \quad L = \frac{5}{6} \quad C = \frac{1}{5}$$

$$p^2 + \frac{1}{RC}p + \frac{1}{LC} = 0$$

$$p^2 + \frac{1}{5}p + \frac{6}{5} = 0$$

1. 判断下图电路过渡过程的性质。(过阻尼, 欠阻尼, 临界阻尼)

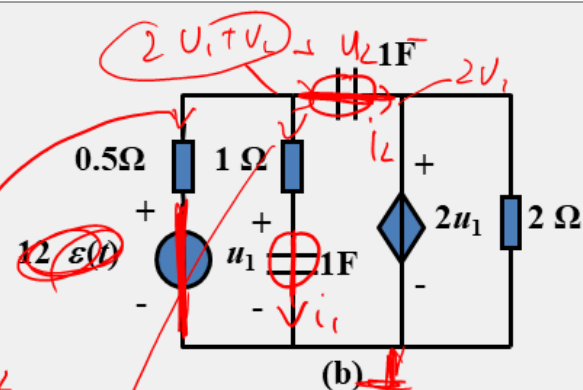


$$\begin{pmatrix} \dot{u}_1 \\ \dot{u}_2 \end{pmatrix} = \begin{pmatrix} 1 & 1 \\ -5 & -3 \end{pmatrix} \begin{pmatrix} u_1 \\ u_2 \end{pmatrix}$$

$$(\lambda + 1)^2 + 1^2 = 0$$

$$\lambda_{1,2} = -1 \pm j \quad \underline{\underline{\text{欠}}}$$

2. 列写以 u_C 、 i_{L1} 和 i_{L2} 为状态变量的状态方程

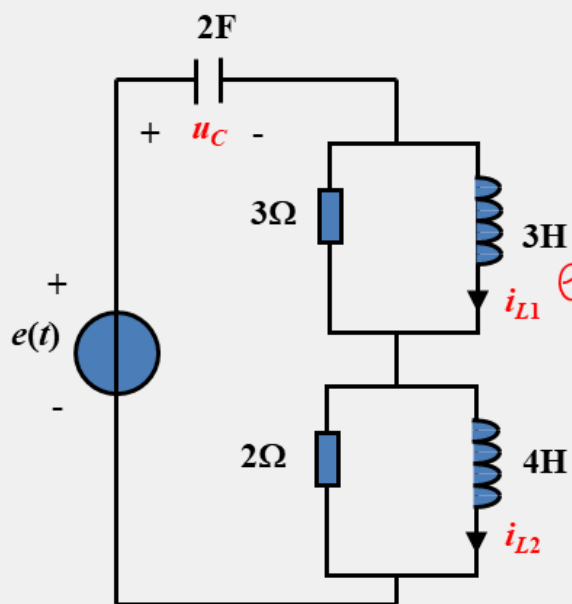

Handwritten derivation of the state equations:

Node voltage u_1 is defined at the node after the capacitor. Node voltage u_2 is defined at the node after the second parallel branch.

Currents are labeled: i (current from capacitor), i_1 (current through 3Ω resistor), i_2 (current through 2Ω resistor).

Equations derived:

$$\left(\frac{1}{3} + \frac{1}{2} \right) u_2 - \frac{1}{3} (e - u_C) = i_1 - i_2$$

$$u_2 = -0.4 u_C + 1.2 i_1 - 0.2 i_2 + 0.4 e$$

$$\begin{pmatrix} \dot{u}_C \\ \dot{i}_1 \\ \dot{i}_2 \end{pmatrix} = \begin{pmatrix} -0.1 & 0.3 & 0.2 \\ -0.2 & -0.4 & 0.4 \\ -0.1 & 0.3 & -0.3 \end{pmatrix} \begin{pmatrix} u_C \\ i_1 \\ i_2 \end{pmatrix} + \begin{pmatrix} 0.1 \\ 0.2 \\ 0.1 \end{pmatrix} e$$

单选题 1分


电流源 $i_s = 2\delta(t)$ A, 计算电感电流 i_L 与电容电压 u_C 零时刻 ($t=0^+$) 的初值 (红包)

A 2, 4





B 0, 2

C 2, 2

D 4, 2

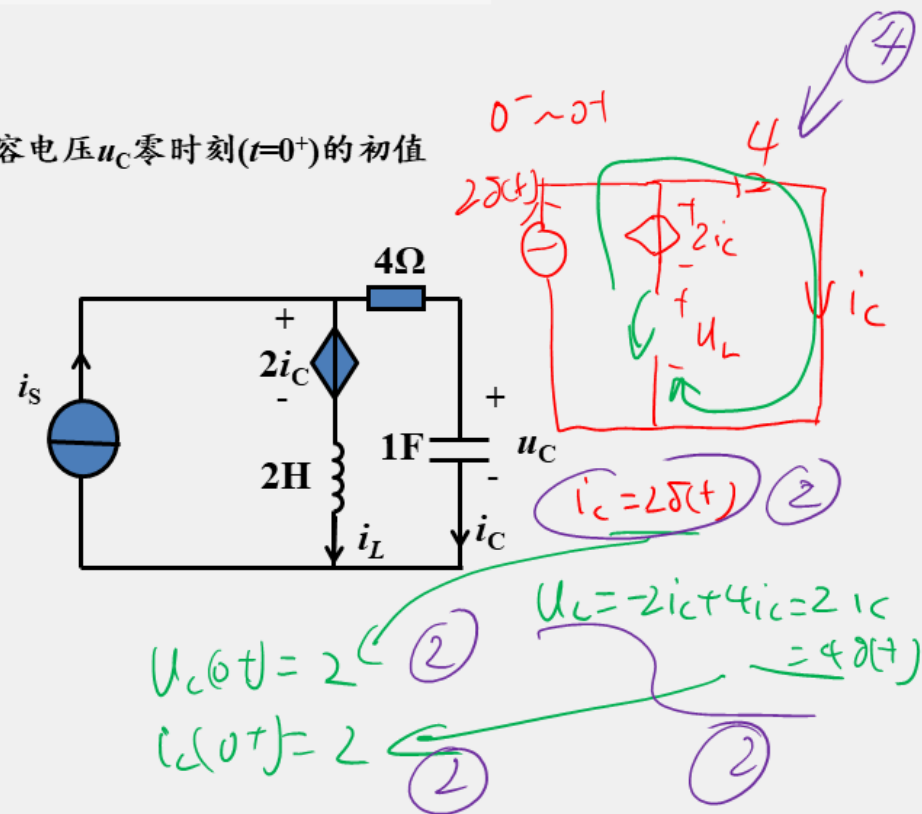

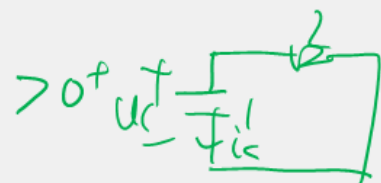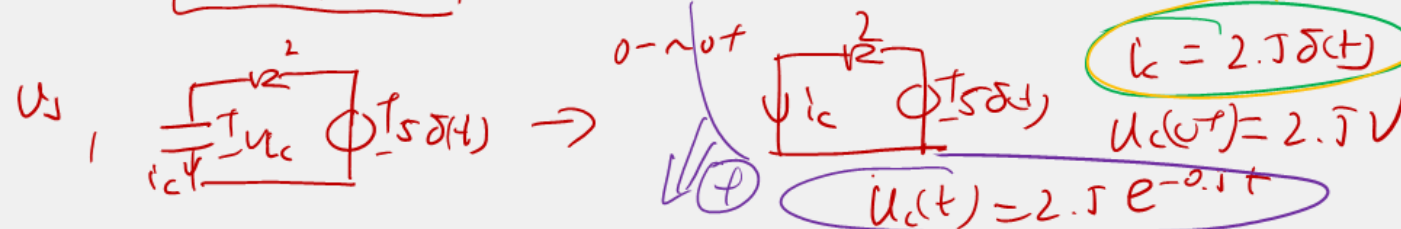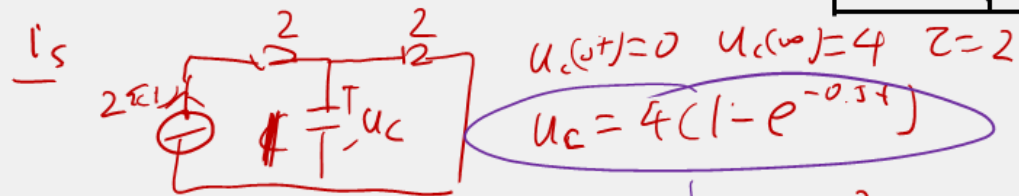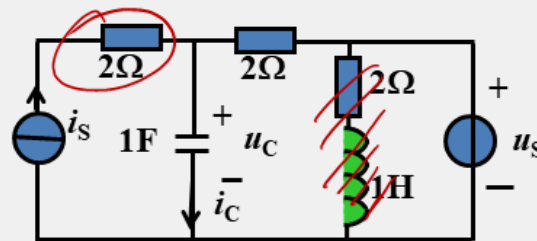3. 已知零状态电路中, 电压源 $u_s = 5\delta(t)$ V,
 电流源 $i_s = 2\delta(t)$ A,
 求: (1) 电容电压 $u_c(t)$
 (2) 电压源 u_s 单独作用时电容电流 $i_c(t)$ 。



$$u_c(t) = 4 - 1.5 e^{-0.5t}$$

$$i_c(0+) = -1.15 \quad i_c(\infty) = 0 \quad i_c(t) = -(1.15 e^{-0.5t}) \delta(t)$$

$$i_c(t) = 2.5 \delta(t) - (1.15 e^{-0.5t}) \delta(t)$$

4. 已知线性网络零输入响应为 $8e^{-t}$ 。当激励 $e(t) = \varepsilon(t)$ 作用时, 网络产生的响应为 $4(1+e^{-t}) \quad t > 0$ 。求当激励 $e(t) = 0.5e^{-3t} \varepsilon(t)$ 作用时网络产生的响应。

① $21R \quad 8e^{-t}$

② $\varepsilon(t)$ 作用 $FR = 21R + 2SR = 4 + 4e^{-t}$

③ $\varepsilon(t)$ 作用 $2SR \quad 4 - 4e^{-t} \rightarrow \frac{(4 - 4e^{-t}) \varepsilon(t)}{f(t) \cdot g(t)}$

④ $h(t): 4e^{-t} \varepsilon(t)$

⑤ $2SR \quad \int_0^+ 0.5e^{-3\tau} 4e^{-(t-\tau)} d\tau$
 $= 2e^{-t} \int_0^+ e^{-2\tau} d\tau = (e^{-t} - e^{-3t}) \varepsilon(t)$


$(4 - 4e^{-t}) \delta(t)$
 $f(t) \cdot \delta(t)$
 $= f(0) \cdot \delta(t)$


⑥ $0.5e^{-3t}$
 $FR = 2SR + 21R = (9e^{-t} - e^{-3t}) \varepsilon(t)$

5. 已知 $e(t)$ 如图, $R=1\Omega$, $C=1F$,
用卷积积分求 $u_C(t)$ 。

(1) $2/R$ $u_C(0^+) = u_C(0^-) = 2$ $u_C(\infty) = 0$ $\tau = 1$
 $u_C(t) = 2e^{-t}$

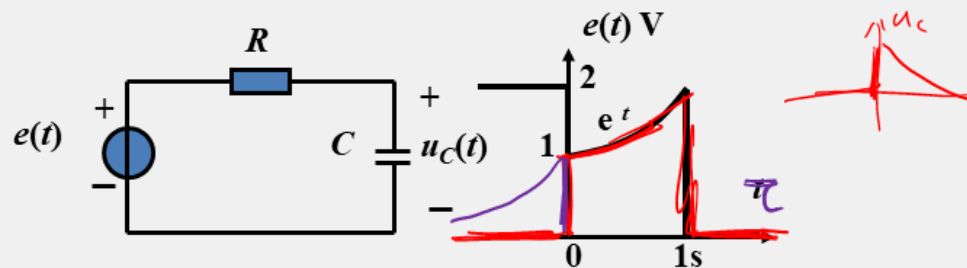(2) $h(t)$ $i_C = \delta(t)$ $u_C(0^+) = 1$ $u_C(\infty) = 0$ $\tau = 1$
 $h(t) = e^{-t}$



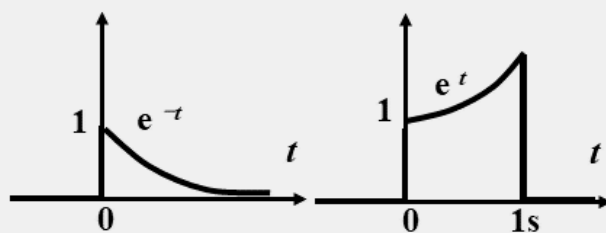


卷积图解法总结

- 什么时候用
 - 被积函数仅在有限时段内有非零函数
- 怎么用
 - 卷、移、乘、积
 - t 轴0点在卷后函数图形的右下角（右移最前沿）
 - t 轴0点和 τ 轴0点定 $\tau \sim t$ 关系
 - 随着 t 值增加，根据公共有值区间划分时段
 - 随着 t 值增加，根据 t 值在 τ 轴上的位置定积分上下限
 - 卷无限时段有非零值的函数相对容易
 - 卷紧贴纵轴的函数相对较容易


6. $C_1 = 4\mu\text{F}$ $C_2 = 2\mu\text{F}$ $R = 1\text{k}\Omega$

$u_{C1}(0^-) = 120\text{V}$ $u_{C2}(0^-) = 0\text{V}$


求: u_{C1} , u_{C2}

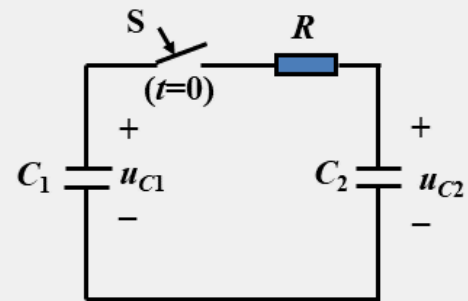


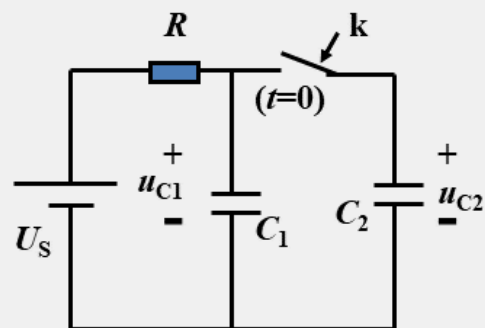7. 已知： C_2 原来未充电， $t=0$ 时合 k 。
求： u_{C1} ， u_{C2} ， i_{C1} ， i_{C2} 。



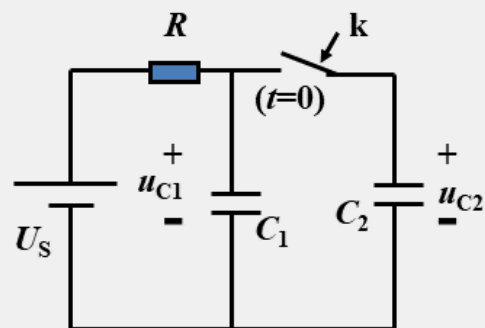7. 已知： C_2 原来未充电， $t=0$ 时合 k 。
求： u_{C1} ， u_{C2} ， i_{C1} ， i_{C2} 。



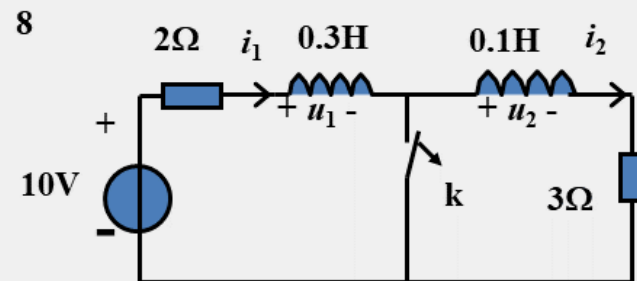

已知如图

求: i_1 , i_2 和 u_1 , u_2 。

动态电路中不同层级的叠加思想

- 列写状态方程的叠加
 - 根据方程进行的叠加
- $ZIR+ZSR$ 的叠加
 - 根据物理性质进行的叠加
- 两个 ε 函数构成一个窗函数的叠加
 - 根据图形进行的叠加