

A 208-V four-pole 60-Hz Y-connected wound-rotor induction motor is rated at 30 hp. Its equivalent circuit components are

$$R_1 = 0.100 \, \Omega \quad R_2 = 0.070 \, \Omega \quad X_M = 10.0 \, \Omega$$

$$X_1 = 0.210 \, \Omega \quad X_2 = 0.210 \, \Omega$$

$$P_{\text{mech}} = 500 \, \text{W} \quad P_{\text{misc}} \approx 0 \quad P_{\text{core}} = 400 \, \text{W}$$

For a slip of 0.05, find

- (a) The line current I_L
- (b) The stator copper losses P_{SCL}
- (c) The air-gap power P_{AG}
- (d) The power converted from electrical to mechanical form P_{conv}
- (e) The induced torque τ_{ind}
- (f) The load torque τ_{load}
- (g) The overall machine efficiency
- (h) The motor speed in revolutions per minute and radians per second