

1.

The following information is given about the simple rotating loop shown in Figure 7-6:

$$B = 0.4 \text{ T}$$

$$V_B = 48 \text{ V}$$


$$l = 0.5 \text{ m}$$

$$R = 0.4 \Omega$$


$$r = 0.25 \text{ m}$$

$$\omega = 500 \text{ rad/s}$$

- Is this machine operating as a motor or a generator? Explain.
- What is the current i flowing into or out of the machine? What is the power flowing into or out of the machine?
- If the speed of the rotor were changed to 550 rad/s, what would happen to the current flow into or out of the machine?
- If the speed of the rotor were changed to 450 rad/s, what would happen to the current flow into or out of the machine?

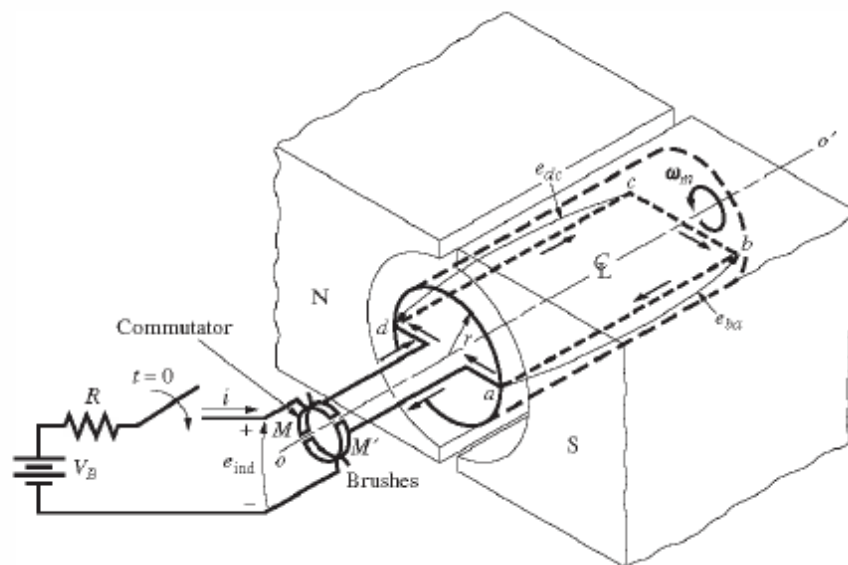

(a)

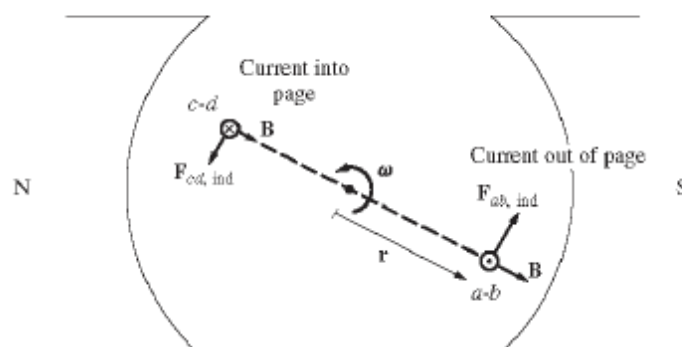

(b)

FIGURE 7-6

Derivation of an equation for the induced torque in the loop. Note that the iron core is not shown in part b for clarity.

2.

A 208-V six-pole Y-connected 25-hp design class B induction motor is tested in the laboratory, with the following results:

No load:	208 V, 24.0 A, 1400 W, 60 Hz
Locked rotor:	24.6 V, 64.5 A, 2200 W, 15 Hz
Dc test:	13.5 V, 64 A

Find the equivalent circuit of this motor, and plot its torque-speed characteristic curve.

(or write the torque-speed equation instead of plot the figure)

Homework 14

1. (a)
$$e_{ind} = 2rLBw$$
$$= 2 \times 0.25 \times 0.5 \times 0.4 \times 500$$
$$= 50V$$

$$V_B = 48V \Rightarrow e_{ind} > V_B \therefore \text{generator}$$

(b)
$$\bar{i} = \frac{e_{ind} - V_B}{R}$$
$$= \frac{50 - 48}{0.4}$$
$$= 5A$$
$$P = \bar{i} e_{ind}$$
$$= 5 \times 50$$
$$= 250W$$

(c)
$$e_{ind}' = 2rLBw$$
$$= 2 \times 0.25 \times 0.5 \times 0.4 \times 550$$
$$= 55V$$
$$\therefore \text{generator}$$
$$\bar{i} = \frac{e_{ind} - V_B}{R}$$
$$= \frac{55 - 48}{0.4}$$
$$= 17.5A$$

(d)
$$e_{ind}'' = 2rLBw$$
$$= 2 \times 0.25 \times 0.5 \times 0.4 \times 450$$
$$= 45V$$
$$\therefore \text{motor}$$
$$\bar{i} = \frac{V_B - e_{ind}}{R}$$
$$= \frac{48 - 45}{0.4}$$
$$= 7.5A$$

2. no load test:
$$X_1 + X_m = \frac{\frac{208}{\sqrt{3}}}{24} = 5\Omega$$

lock-rotor test:
$$R_{LR} + jX'_{LR} = \frac{\frac{24.6}{\sqrt{3}}}{64.5} = 0.22\Omega$$

$$\theta'_{LR} = \cos^{-1} \frac{2200}{\sqrt{3} \times 24.6 \times 64.5} = 36.82^\circ$$

$$R_{LR} = R_1 + R_2 = |Z'_{LR}| \cos \theta_{LR} = 0.22 \times \cos 36.82^\circ = 0.176$$

DC test:
$$R_1 = \frac{1}{2} \frac{13.5}{64} \Rightarrow R_2 = R_{LR} - R_1$$
$$= 0.105\Omega$$
$$= 0.176 - 0.105$$
$$= 0.071\Omega$$

$$X'_{LR} = |Z'_{LR}| \sin \theta_{LR} = 0.22 \sin 36.82^\circ = 0.528\Omega$$

Design Class 13 motor: $X_1 = 0.211\Omega$, $X_2 = 0.317\Omega$

$$\begin{aligned}\therefore X_m &= 5 - X_1 \\ &= 5 - 0.211 \\ &= 4.789\Omega\end{aligned}$$

equivalent circuit:

