A 208-V four-pole 60-Hz Y-connected wound-rotor induction motor is rated at 30 hp. Its equivalent circuit components are

$$R_1 = 0.100 \; \Omega \hspace{1cm} R_2 = 0.070 \; \Omega \hspace{1cm} X_M = 10.0 \; \Omega$$

$$X_1 = 0.210 \Omega$$
 $X_2 = 0.210 \Omega$

$$P_{\mathrm{mech}} = 500 \; \mathrm{W}$$
 $P_{\mathrm{misc}} \approx 0$ $P_{\mathrm{core}} = 400 \; \mathrm{W}$

For a slip of 0.05, find

- (a) The line current I_L
- (b) The stator copper losses $P_{\rm SCL}$
- (c) The air-gap power $P_{\rm AG}$
- (d) The power converted from electrical to mechanical form P_{conv}
- (e) The induced torque $\tau_{\rm ind}$
- (f) The load torque $\tau_{\rm load}$
- (g) The overall machine efficiency
- (h) The motor speed in revolutions per minute and radians per second



